

DHDL

The D Hardware Design Language

Luís Marques
[<luis@luismarques.eu>](mailto:luis@luismarques.eu)



<http://live.dhlang.org>

What is hardware?

What is hardware?

You compile this code with DMD:

```
uint mul(uint a, uint b)
{
    return a * b;
}
```

Question 1:

Is this multiplication implemented in hardware?
(i.e., is it hardware accelerated?)

What is hardware?

Question 2:

What about this one?

```
uint mul(uint a, uint b)
{
    uint sum = 0;

    while(a != 0)
    {
        if((a & 1) != 0)
            sum += b;

        b <<= 1;
        a >>= 1;
    }

    return sum;
}
```

What is hardware?

You compile this code with ~~DMD~~ DMC


```
uint mul(uint a, uint b)
{
    return a * b;
}
```

...and you run it on an original Intel 8086.

Question 3:

Is this multiplication implemented in hardware?

What is hardware?

 

```
uint mul(uint a, uint b)
{
    uint sum = 0;

    while(a != 0)
    {
        if((a & 1) != 0)
            sum += b;

        b <<= 1;
        a >>= 1;
    }

    return sum;
}
```

- Each 8086 instruction is executed as n μinstructions
- What if I tell you that the μcode for the **mul** instruction executes *this* algorithm?
- **Question 4:** Is the **mul** instruction implemented in HW?


What is hardware?

- What if there is no µcode, but the multiplication circuit works through a series of additions and shifts?
- **Question 5:** Does it make a difference? Is it (still?) hardware?


What is hardware?

- Software
 - Dynamic allocation of resources
 - Generic
 - Flexible
 - Serial
- Hardware
 - Fixed resources for each function
 - Specialized
 - Hardcoded
 - Parallel

Why Hardware Matters

 

Why Hardware Matters


 


Why Hardware Matters

- Clock frequency has stopped increasing
 - Solutions:
 - Multiple cores
 - GPUs
 - FPGAs
 - ASICs
- 
- +parallel
+specialized
+harder

Why Hardware Matters

  - The datacenter doesn't lie
- E.g., Amazon
 - GPU instances
 - FPGA instances (f1)



Creating Hardware

Creating Hardware

```
import core.stdio.stdio;  
  
void main()  
{  
    int a, op, b, v;  
  
    while(true)  
    {  
        a = getchar();  
        op = getchar();  
        b = getchar();  
        if(op == '+') v = a+b-'0';  
        if(op == '-') v = a-b+'0';  
        putchar(v);  
        putchar('\n'); getchar();  
    }  
}
```

```
$ rdmd -version=v1 calc.d  
3+4  
7  
8-5  
3
```

Creating Hardware

```
import core.stdio.stdio;  
  
void main()  
{  
    int a, op, b, v, ip;
```

```
    while(true)  
    {  
        if(ip == 0) { a = getchar(); ++ip; }  
        if(ip == 1) { op = getchar(); ++ip; }  
        if(ip == 2) { b = getchar(); ++ip; }  
        if(ip == 3) { if(op == '+') v = a+b-'0'; ++ip; }  
        if(ip == 4) { if(op == '-') v = a-b+'0'; ++ip; }  
        if(ip == 5) { putchar(v); ++ip; }  
        if(ip == 6) { putchar('\n'); getchar(); ip=0; }  
    }  
}
```

```
$ rdmd -version=v2 calc.d  
3+4  
7  
8-5  
3
```

Creating Hardware

```
int a, op, b, v, ip;

while(true)
{
    ip0:   if(ip == 0) { a = getchar(); ++ip; goto d; }
    ip1:   if(ip == 1) { op = getchar(); ++ip; goto d; }
    ip2:   if(ip == 2) { b = getchar(); ++ip; goto d; }
    ip3:   if(ip == 3) { if(op == '+') v = a+b-'0'; ++ip; goto d; }
    ip4:   if(ip == 4) { if(op == '-') v = a-b+'0'; ++ip; goto d; }
    ip5:   if(ip == 5) { putchar(v); ++ip; goto d; }
    ip6:   if(ip == 6) { putchar('\'n'); getchar(); ip=0; goto d; }

d:    final switch(uniform(0, 7))
{
    case 0: goto ip0;
    case 1: goto ip1;
    case 2: goto ip2;
    case 3: goto ip3;
    case 4: goto ip4;
    case 5: goto ip5;
    case 6: goto ip6;
}
```

```
$ rdmd -version=v3 calc.d
3+4
7
8-5
3
```

Creating Hardware

```
import core.stdio.stdio;  
  
void main()  
{  
    int a, op, b, v, ip;
```

```
    while(true)  
    {  
        if(ip == 0) { a = getchar(); ++ip; }  
        if(ip == 1) { op = getchar(); ++ip; }  
        if(ip == 2) { b = getchar(); ++ip; }  
        if(ip == 3) { if(op == '+') v = a+b-'0'; ++ip; }  
        if(ip == 4) { if(op == '-') v = a-b+'0'; ++ip; }  
        if(ip == 5) { putchar(v); ++ip; }  
        if(ip == 6) { putchar('\n'); getchar(); ip=0; }  
    }  
}
```

```
$ rdmd -version=v2 calc.d  
3+4  
7  
8-5  
3
```

Creating Hardware

```
import core.stdio.stdio;

void main()
{
    int a, op, b, v, ip;

    while(true)
    {
        ip = (ip + 1) % 7;
        if(ip == 0) a = getchar();
        if(ip == 1) op = getchar();
        if(ip == 2) b = getchar();
        if(ip == 3) if(op == '+') v = a+b-'0';
        if(ip == 4) if(op == '-') v = a-b+'0';
        if(ip == 5) putchar(v);
        if(ip == 6) putchar('\'\n'); getchar();
    }
}
```

Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

    while(true)
    {
        ip = (ip + 1) % 5;
        if(ip == 0) a = getchar();
        if(ip == 1) op = getchar();
        if(ip == 2) b = getchar();
        if(ip == 3) if(op == '+') v = a+b-'0';
        if(ip == 4) if(op == '-') v = a-b+'0';
    }
}
```

Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = getchar();
        if(ip == 1) op = getchar();
        if(ip == 2) b = getchar();
        if(ip == 3) op == '+' ? v = a+b-'0' : v = a-b+'0';
    }
}
```

Creating Hardware

```
void main()  
{  
    int a, op, b, v, ip;  
  
    while(true)  
    {  
        ip = (ip + 1) % 4;  
        if(ip == 0) a = input();  
        if(ip == 1) op = input();  
        if(ip == 2) b = input();  
        if(ip == 3) op == 0 ? v = a+b : v = a-b;  
    }  
}
```

Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```

adder subcircuit

Creating Hardware

```
void main()
{
    int a, op, b, v, ip;


    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```

addition subcircuit

Question 6: How many subcircuits are there in here?

Creating Hardware

```
void main()
{
    int a, op, b, v, ip;
```

 


Question 6: How many subcircuits are there in here?

Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

 
    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```



Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

 
    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```



Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

 
    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```



Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

 
    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```



Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

 
    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```



Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

 
    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```



Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

 
    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```



Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

     while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```




Creating Hardware

```

void main()
{
    int a, op, b, v, ip;

    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}

```

 


Creating Hardware

```

void main()
{
    int a, op, b, v, ip;

    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}

```

 


Creating Hardware

```

void main()
{
    int a, op, b, v, ip;

    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}

```

 


Creating Hardware

```

void main()
{
    int a, op, b, v, ip;

    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}


```

 

Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

 
    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```



Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

 
    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```



Creating Hardware

```
void main()
{
    int a, op, b, v, ip;


 
    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```



Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

 
 
    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```



Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

 
 
    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```



Creating Hardware

```
void main()
{
    int a, op, b, v, ip;

 
 
    while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```




Creating Hardware


```
void main()
{
    int a, op, b, v, ip;

      while(true)
    {
        ip = (ip + 1) % 4;
        if(ip == 0) a = input();
        if(ip == 1) op = input();
        if(ip == 2) b = input();
        if(ip == 3) op == 0 ? v = a+b : v = a-b;
    }
}
```



(one-hot encoding)

 

 


Question 7: There's an important optimization left to do in this circuit. What is it?


Question 7

- Optimization: $-x == \sim x + 1; a+b == a+(\sim b)+1$

if(ip == 3) op == 0 ? v = a+b : v = a-b;

 

if(ip == 3) v = a + (op == 0 ? b : ~b) + 1;

 

Question 8

- **Question 8:** do you know what an exclusive or (XOR) is?

[] Yes

[] No

[] Is this a trick question?

Question 8

- **Question 8:** do you know what an exclusive or (XOR) is?

[] Yes


[] No


[] Is this a trick question?

invert B?

```
if(ip == 3) v = a + (op == 0 ? b : ~b + 1);
```

INPUT		OUTPUT
A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

 


 

Creating Hardware

- Approach 1: Describe the algorithm, derive the circuit from the description (high level synthesis)
 
```
int a, op, b, v;  
  
while(true)  
{  
    a = getchar();  
    op = getchar();  
    b = getchar();  
    if(op == '+') v = a+b-'0';  
    if(op == '-') v = a-b+'0';  
    putchar(v);  
    putchar('\n'); getchar();  
}
```




Creating Hardware

- Approach 2: Write an event-based simulation of your design. Let the tools infer what hardware would be consistent with that simulation.
 - In practise, only the simulations for which there is an obvious mapping to hardware work. That's the so-called synthesizable subset.

Creating Hardware

- Approach 3: Describe the circuit (RTL generator)
 
```
void main()
{
    auto a = new Reg();
    auto op = new Reg();
    auto b = new Reg();
    auto ip = new Reg();
    auto adder = new Adder;
    adder.connect(a, b);
    auto dec = new Decoder();
    dec.connect(ip);
    // ... etc
}
```



Creating Hardware

- Approach 1: High-level synthesis
Approach 2: Event-based
Approach 3: RTL builder
- VHDL & Verilog: Follow mostly approach 2
- DHDL (and Chisel, SpinalHDL, etc.): Follows mostly approach 3
- Not pure: You don't have to specify events / gates for combinational circuits, just write $(a + b) * 7$ etc.

DHDL

- What is DHDL?
 - A hardware design language
 - D Language extension + D library
 - Falls more on the RTL generator side (currently)
- Why DHDL?
 - Modern design

Modern Design

- `int sum(int[] values);` Level 0: one tool does one job
- `int mul(int[] values);` Level 0: one tool does one job
- `auto accumulate(alias op, T)(T[] values);`
 - Level 1: one tool does multiple jobs
 - Level 1: generates multiple tools, each of which do one job

Modern Design

Question 9:

At what level do hardware designers work?

Level -1

(sometimes...)

Modern Design

- Level -1:
- Level 0: one tool does one job
(e.g. max computes maximums)
- Level 1: one tool does multiple jobs
(e.g. accumulate computes sums, maximums, etc.)

Modern Design

- Level -1: multiple tools needed to do one job
(`sum_part1()`, `sum_part2()`?)
- Level 0: one tool does one job
(e.g. `max` computes maximums)
- Level 1: one tool does multiple jobs
(e.g. `accumulate` computes sums, maximums, etc.)

HDL Woes

- VHDL was created to create simulations of hardware
- After debugging the design, the hardware was built by converting to a schematic, where you wired simple gates, etc.
- Why not make the conversion automatic?
- Hardware engineers were used to schematic entry as a design method. VHDL was nailed with that hammer.
- Lots of little blocks without obvious relationship

HDL Woes

- void sum_part1()
{
 thread
}
- void sum_part2()
{
 thread
}

HDL Woes

```
CBandDatat_LatchPROC9F: process(MDLE, CB_In, Reset_Out_N)
begin
  if Reset_Out_N = '0' then
    CBLatch_F_1      <= "0000";
  elsif MDLE = '1' then
    CBLatch_F_1      <= CB_In(3 downto 0);
  end if;
end process;

CBandDatat_LatchPROC10F: process(MDLE, CB_In, DParIO_In, Reset_Out_N)
begin
  if Reset_Out_N = '0' then
    CBLatch_F_2      <= "0000";
  elsif MDLE = '1' then
    CBLatch_F_2(6 downto 4) <= CB_In(6 downto 4);
    CBLatch_F_2(7)       <= DParIO_In;
  end if;
end process;

CBLatch_F <= CBLatch_F_2 & CBLatch_F_1;

BullEn_PROC: process(Mem_Test, ByteSel)
begin
  BullEn <= not (ByteSel(0) and ByteSel(1) and ByteSel(2) and ByteSel(3)) or Mem_Test;
end process;

IUCHk_Out_Gen: process (IUDataLatch_F, ChkGen_Data, BullEn, CB_bull)
  Variable IUGen_Chk : std_logic_vector(7 downto 0);

begin
  IUGen_Chk(6 downto 0) := ChkGen (IUDataLatch_F);
  IUGen_Chk(7)          := ChkGen_Data(32);
  CB_Out_Int <= mux2 (BullEn, IUGen_Chk, CB_bull);
end process;
```

HDL Woes

- The argument is:
 - VHDL was originally created for simulation
 - Synthesis was added later
 - Problems arose from that
- But then at least things related to simulation should be pretty good, right?

HDL Woes

```
entity hello_world is
end hello_world;

architecture behaviour of hello_world is
    signal foo : std_logic;
begin
    process begin
        foo <= '1';
        wait for 1 ns;
        report std_logic'image(foo);
        foo <= '0';
        wait for 1 ns;
        report std_logic'image(foo);
        wait;
    end process;
end behaviour;
```

```
$ ghdl -a hello.vhdl && ghdl -e hello_world
$ ./hello_wold
hello.vhdl:13:8:@1ns:(report note): '1'
hello.vhdl:16:8:@2ns:(report note): '0'
```


HDL Woes

```
entity hello_world is  
end hello_world;
```

```
architecture behaviour of hello_world is  
    signal foo : std_logic_vector(7 downto 0);  
begin  
    process begin  
        foo <= "11111111";  
        wait for 1 ns;  
        report std_logic_vector'image(foo);  
        foo <= "00000000";  
        wait for 1 ns;  
        report std_logic_vector'image(foo);  
        wait;  
    end process;  
end behaviour;
```

```
$ ghdl -a hello.vhdl && ghdl -e hello_world  
hello.vhdl:13:32: prefix of 'image'  
attribute must be a scalar type  
hello.vhdl:13:32: found array type  
"std_logic_vector" defined at ../../src/  
ieee/std_logic_1164.v93:69:30
```

HDL Woes

 



vhdl print std_logic_vector



All

Images

News

Videos

More

Settings

Tools

About 11,300 results (0.68 seconds)

How to Display std_logic_vector Value? - Google Groups

<https://groups.google.com/d/topic/comp.lang.vhdl/ZkyIUFluj4> ▾

Jan 15, 2001 - comp.lang.vhdl › ... How can I display the value of std_logic_vector? ... a) Both compilers complain data_out is incorrect type for REPORT.

VHDL BLOG: Print to STDOUT using REPORT Statement in VHDL

sagekingthegreat.blogspot.com/2013/08/report-statement-report-statement-is.html ▾

Aug 12, 2013 - variable B : std_logic := '1'; report "B value is" & std_logic'image(B); output > B value is 1. (C) To print std_logic_vector type values to STDOUT ...

How do I use VHDL write() function to print std_logic_vector type ...

www.edaboard.com › ... › PLD, SPLD, GAL, CPLD, FPGA Design

May 23, 2012 - 3 posts - 2 authors

Can anyone tell me how to do it? I used to use report() function, but recently learned that write() can be used for printing things on a screen.

how to write ucf file in xilinx for vhdl code for an ... 6 posts 28 Apr 2014

[SOLVED] decimal numbers in vhdl - EDA Board 12 posts 3 Aug 2011

More results from www.edaboard.com

How to print std_logic_vector variable into hex string in VHDL ...

[https://www.thecodingforums.com](http://www.thecodingforums.com) › Archive › Archive › VHDL

Aug 31, 2005 - 5 posts - 4 authors

How to print std_logic_vector variable into hex string in VHDL ... Is there any command like "report integer'image(myvalue)"; so that it will print ...

vhdl - Is there a way to print the values of a signal to a file from a ...

[stack overflow.com/.../is-there-a-way-to-print-the-values-of-a-signal-to-a-file-from-a-](http://stackoverflow.com/.../is-there-a-way-to-print-the-values-of-a-signal-to-a-file-from-a-...) ... ▾

Jun 20, 2014 - First make functions that convert std_logic and std_logic_vector to string like: function to_bstring(sl : std_logic) return string is variable sl_str_v ...



pin...@my-deja.com

1/16/01



You may want use this function:

```
-- By PK debug mean for printing std_logic
function prtstd( v : std_logic_vector ) return integer is
variable s : string( 3 downto 1 );
variable r : string( (v'left+1) downto (v'right+1) );
begin
  for i in v'left downto v'right loop
    --report std_logic'image(v(i));
    s := std_logic'image(v(i));
    --string must start/stop at 1
    --      '1' we need only the second character
    r(i+1) := s(2);
  end loop;
  report "dbg by pk " & r & " dbg end";
  return 0;
end prtstd;
```

Call it by:

```
junk := prtstd( FileDesc.CurrentWord );
```

In article <940isc\$qfe\$1...@nnrp1.deja.com>,

- show quoted text -



vhdl print std_logic_vector



All Images News Videos More

Settings Tools

About 11,300 results (0.68 seconds)

How to Display std_logic_vector Value? - Google Groups

<https://groups.google.com/d/topic/comp.lang.vhdl/ZkyIUFluj4> ▾

Jan 15, 2001 - comp.lang.vhdl › ... How can I display the value of std_logic_vector? ... a) Both compilers complain data_out is incorrect type for REPORT.

VHDL BLOG: Print to STDOUT using REPORT Statement in VHDL

sagekingthegreat.blogspot.com/2013/08/report-statement-report-statement-is.html ▾

Aug 12, 2013 - variable B : std_logic := '1'; report "B value is" & std_logic'image(B); output > B value is 1. (C) To print std_logic_vector type values to STDOUT ...

How do I use VHDL write() function to print std_logic_vector type ...

www.edaboard.com › ... › PLD, SPLD, GAL, CPLD, FPGA Design

May 23, 2012 - 3 posts - 2 authors

Can anyone tell me how to do it? I used to use report() function, but recently learned that write() can be used for printing things on a screen.

how to write ucf file in xilinx for vhdl code for an ... 6 posts 28 Apr 2014

[SOLVED] decimal numbers in vhdl - EDA Board 12 posts 3 Aug 2011

More results from www.edaboard.com

How to print std_logic_vector variable into hex string in VHDL ...

[https://www.thecodingforums.com](http://www.thecodingforums.com) › Archive › Archive › VHDL

Aug 31, 2005 - 5 posts - 4 authors

How to print std_logic_vector variable into hex string in VHDL ... Is there any command like "report integer'image(myvalue)"; so that it will print ...

vhdl - Is there a way to print the values of a signal to a file from a ...

stackoverflow.com .../is-there-a-way-to-print-the-values-of-a-signal-to-a-file-from-a-...

Jun 20, 2014 - First make functions that convert std_logic and std_logic_vector to string like: function to_bstring(sl : std_logic) return string is variable sl_str_v ...

HDL Woes

▲
3
▼

As you have discovered, the 'image attribute is only declared for scalar types, not arrays or records : the usual approach is to create one's own library of test utilities including `to_string` or `image` functions in a package at the start of a design, and use it throughout.

It would be perfectly possible to standardise a library of these, and you will probably find many potential "test utility" packages but none has really caught on well enough to deserve becoming a standard.

That being said, you might find the following package a useful starting point.

- wat?
- Is this what the competition looks like?
You have to create your own writeln?

HDL Woes

- More seriously, here are the fundamental problems:
 - VHDL & Verilog are event-based
 - Only a subset is synthesizable
 - Only a subset of that subset actually works in practise.
 - Which sub-sub-set? Oh, it depends on the tool vendor!
 - No OOP, FP or generics. Everything is verbose, repetitive and error prone

HDL Woes

- Only VHDL and Verilog are mainstream, but there are some competitors:
 - Bluespec, Lava, Hydra, ForSyDe, etc. (Haskell)
 - Chisel / SpinalHDL (Scala)
 - MyHDL (Python)
 - CLaSH
 - Lucid

Why DHDL

- DHDL
 - Chisel's hardware construction model...
 - ...without the Scala DSL tax
 - ...with D's modeling power

Why DHDL

- Scala DSL tax

```
if(a == false)
  b := 42;
else
  c := 0;
```


(DHDL)

```
when(a === false.B)
{
  b := 42.U
}
.otherwise
{
  c := 0.U
}
```

(Chisel)


Why DHDL

- Compiling DHDL

 


Why DHDL

- Compiling DHDL

 


DHDL

- What we'll see today


 


FPGA

 - What's an FPGA?
 - The largest VLIW CPU in the world
 - An interpreter for hardware




(VLIW)


 
 


(FPGA)

FPGA

 


FPGA

  
 


FPGA

 - We'll be using a Papilio Pro in this talk




Papilio Wings

  

Papilio Wings


GND	0
	1
3V3	2
5V	3
	4
	5
	6
	7

GND	0
	1
3V3	2
5V	3
	4
	5
	6
	7

 


Papilio Wings

GND	0
	1
3V3	2
5V	3
	4
	5
	6
	7
GND	8
	9
3V3	10
5V	11
	12
	13
	14
	15

 

	C
GND	0
	1
3V3	2
5V	3
	4
	5
	6
	7
GND	8
	9
3V3	10
5V	11
	12
	13
	14
	15

	B	A
GND	0	15
	1	14
3V3	2	13
5V	3	12
	4	11
	5	10
	6	9
	7	8
GND	8	7
	9	6
3V3	10	5
5V	11	4
	12	3
	13	2
	14	1
	15	0
		GND

 




Papilio Wings

A-B-C x 2

GND	0
	1
3V3	2
5V	3
	4
	5
	6
	7




Audio

 

Buttons+LEDs




Joystick

 

SD Card



VGA

 


Wii Controller



Papilio Wings

C


GND	0
	1
3V3	2
5V	3
	4
	5
	6
	7
GND	8
	9
3V3	10
5V	11
	12
	13
	14
	15

 

Breadboard

A


15	
14	
13	
12	
11	5V
10	3V3
9	
8	GND
	7
	6
	5
	4
3	5V
2	3V3
1	
0	GND

 


I/O Buffer
(Logic Analyser)




Papilio MegaWings

 

LogicStart

 


RetroCade

 


Arcade



 
How to Win an FPGA and Influence Hardware



LogicStart

 

Papilio Pro

 

Wings

Hello World

helloworld.dhdl

```
circut HelloWorld
{
    port in bool a;
    port out bool b;


    b := a;
}
```

Hello World

helloworld.dhdl

```
circuit HelloWorld
{
    port in bool a;
    port out bool b;

    b := a;
}
```

 

Hello World

helloworld.dhdl

```
circuit HelloWorld
{
    port in bool a;
    port out bool b;

    b := a;
}
```

```
unittest
{
    auto hello = peekPokeTester!HelloWorld;

    hello.a = false;
    hello.eval();
    assert(hello.b == false);

    hello.a = true;
    hello.eval();
    assert(hello.b == true);
}
```

Hello World

helloworld.dhdl

```
circuit HelloWorld
{
    port in bool a;
    port out bool b;

    b := a;
}
```

HelloWorld.d

```
class HelloWorld : Circuit
{
    Bool a;
    Bool b;

    this()
    {
        a = input("a", new Bool);
        b = output("b", new Bool);

        assign(b, a);
    }
}
```

Hello World

HelloWorld.fir

```
circuit HelloWorld :  
    module HelloWorld :  
        input reset : UInt<1>  
        input clock : Clock  
        input a : UInt<1>  
        output b : UInt<1>  
  
        b is invalid  
  
        b <= a
```

HelloWorld.d

```
class HelloWorld : Circuit  
{  
    Bool a;  
    Bool b;  
  
    this()  
    {  
        a = input("a", new Bool);  
        b = output("b", new Bool);  
  
        assign(b, a);  
    }  
}
```

Hello World

HelloWorld.fir

```
circuit HelloWorld :  
    module HelloWorld :  
        input reset : UInt<1>  
        input clock : Clock  
        input a : UInt<1>  
        output b : UInt<1>  
  
        b is invalid  
  
        b <= a
```

HelloWorld.v

```
module HelloWorld(  
    input  reset,  
    input  clock,  
    input  a,  
    output b  
);  
    assign b = a;  
endmodule
```

Hello World

VHelloWorld.h

```
VL_MODULE(VHelloWorld) {
public:
    VL_IN8(reset,0,0);
    VL_IN8(clock,0,0);
    VL_IN8(a,0,0);
    VL_OUT8(b,0,0);
    (...)
```

VHelloWorld.cpp

```
(...)
```

VHelloWorld (shared library)

```
(...)
```

dhdl\testing.d

```
(...)
```

```
auto r = ctRegex!r"\s*VL_( [A-Z]+[0-9]* )\(( [a-z]+ ),( [0-9]+ ),";
```

HelloWorld.v

```
module HelloWorld(
    input  reset,
    input  clock,
    input  a,
    output b
);
    assign b = a;
endmodule
```

Hello World

helloworld.dhdl

```
circuit HelloWorld
{
    port in bool a;
    port out bool b;

    b := a;
}
```

```
unittest
{
    auto hello = peekPokeTester!HelloWorld;

    hello.a = false;
    hello.eval();
    assert(hello.b == false);

    hello.a = true;
    hello.eval();
    assert(hello.b == true);
}
```

Hello World

helloworld.dhdl

```
circuit HelloWorld
{
    port in bool a;
    port out bool b;

    b := a;
}
```

HelloWorld.v

```
module HelloWorld(
    input    reset,
    input    clock,
    input    a,
    output   b
);
    assign b = a;
endmodule
```


helloworld.ucf

```
NET a LOC="P47" | IOSTANDARD=LVttl;
NET b LOC="P112" | IOSTANDARD=LVttl;
```



button

LED₁



Hello World

 



Hello World

  



Hello World

  



Hello World

  

Hello World

  

Hello World

  

Hello World

Processes: HelloWorld - behavioral

- Design Summary/Reports
- Design Utilities
- User Constraints
- Synthesize - XST
 - View RTL Schematic
 - View Technology Schematic
 - Check Syntax
 - Generate Post-Synthesis Simulation
- Implement Design
 - Translate
 - Map
 - Place & Route
 - Generate Programming File
- Configure Target Device
- Analyze Design Using ChipScope

Papilio Loader 2.8

File Help <http://papilio.cc>

Target Information

Target board: Auto-detect onboard FPGA device

Target .bit file: C:\demo\helloworld.bit


Board Name:

Write to: FPGA

Information

```
Bitstream length: 2724832 bits
Uploading "C:\demo\helloworld.bit". DNA is 0x995f1923bee3caff
Done.
Programming time 578.5 ms
USB transactions: Write 176 read 8 retries 0
```

Hello World

 


Operators

operators.dhdl

```
circuit Operators
{
    port in bool a;
    port in bool b;
    port out bool c;

    b := a & b;
}
```

 

Operators

operators.dhdl

```
circuit Operators
{
    port in bool a;
    port in bool b;
    port out bool c;

    b := a & b;
}
```

```
unittest
{
    auto op = peekPokeTester!Operators;

    op.a = false;
    op.b = true;
    op.eval();
    assert(op.c == false);

    op.a = true;
    op.eval();
    assert(op.c == true);
}
```

Operators

operators.dhdl

```
circuit Operators
{
    port in bool a;
    port in bool b;
    port out bool c;

    b := a & b;
}
```

Operators.d

```
class Operators : Circuit
{
    Bool a;
    Bool b;
    Bool c;

    this()
    {
        a = input("a", new Bool);
        b = input("b", new Bool);
        c = output("c", new Bool);

        assign(c, a.and(b));
    }
}
```

Operators

Operators.fir

```
circuit Operators :  
    module Operators :  
        input reset : UInt<1>  
        input clock : Clock  
        output c : UInt<1>  
        input a : UInt<1>  
        input b : UInt<1>  
  
        c is invalid  
  
        node _T_14 = and(a, b)  
        c <= _T_14
```

Operators.d

```
class Operators : Circuit  
{  
    Bool a;  
    Bool b;  
    Bool c;  
  
    this()  
    {  
        a = input("a", new Bool);  
        b = input("b", new Bool);  
        c = output("c", new Bool);  
  
        assign(c, a.and(b));  
    }  
}
```

Operators


Operators.fir

```
circuit Operators :  
    module Operators :  
        input reset : UInt<1>  
        input clock : Clock  
        output c : UInt<1>  
        input a : UInt<1>  
        input b : UInt<1>  
  
        c is invalid  
  
        node _T_14 = and(a, b)  
        c <= _T_14
```

Operators.v

```
module Operators(  
    input  reset,  
    input  clock,  
    output c,  
    input  a,  
    input  b  
) ;  
    wire _T_14;  
    assign c = _T_14;  
    assign _T_14 = a & b;  
endmodule
```

Operators

 

State

blink.dhdl

```
circuit Blink
{
    port out bool a;

    reg bool state;

    state := !state;
    a := state;
}
```

State

blink.dhdl

```
circuit Blink
{
    port out bool a;


    reg bool state;

    a := state;
    state := !state;
}
```

State

blink.dhdl

 
```
circuit Blink
{
    port out bool a;
    reg bool state;
    a := state;
    state := !state;
}
```



State

blink.dhdl

 
```
circuit Blink
{
    port out bool a;
    reg bool state;
    a := state;
    state := !state;
}
```



State

blink.dhdl
 
```
circuit Blink
{
    port out bool a;
    reg bool state;
    a := state;
    state := !state;
}
```




State

blink.dhdl

```
circuit Blink
{
    port out bool a;

 
    reg bool state;
    a := state;
    state := !state;
}
```



State

blink.dhdl

```
circuit Blink
{
    port out bool a;
    reg bool state;
    a := state;
    state := !state;
}
```

 


Question 10: Will port a blink?

State

blink.dhdl
 
```
circuit Blink
{
    port out bool a;
    reg bool state;
    a := state;
    state := !state;
}
```



State

blink.dhdl

```
circuit Blink
{
    port out bool a;


    reg bool state;
    a := state;
    state := !state;
}
```

```
unittest
{
    auto blink = peekPokeTester!Blink;


    foreach(i; 0..8)
    {
        assert(blink.a == i % 2);
        blink.step();
    }
}
```

Question 11: Will the LED (on port a) blink?

State

 

State

 

State

blink2.dhdl

```
enum clockRate = 32_000_000;

circuit Blink2
{
    port out bool a;


    reg bool state;
    reg uint counter = clockRate;

    a := state;

    if(counter != 0)
        counter := counter - 1;
    else
    {
        counter := clockRate
        state := !state;
    }
}
```

Question 12: Now, will the LED blink? (at 1 Hz)

State

 

State - width inference

blink2.dhdl

```
enum clockRate = 32_000_000;

circuit Blink2
{
    port out bool a;

    reg bool state;
    reg uint counter = clockRate;

    a := state;

    if(counter != 0)
        counter := counter - 1;
    else
    {
        counter := clockRate
        state := !state;
    }
}
```

State - width inference

blink2.dhdl

```
enum clockRate = 32_000_000;

circuit Blink2
{
    port out bool a;

    reg bool state;
    reg uint!25 counter = clockRate;

    a := state;

    if(counter != 0)
        counter := counter - 1;
    else
    {
        counter := clockRate
        state := !state;
    }
}
```

State - width inference

blink2.dhdl

```
enum clockRate = 32_000_000;


circuit Blink2
{
    port out bool a;

    reg bool state;
    reg uint!(clockRate.log2Up) counter = clockRate;


    a := state;

    if(counter != 0)
        counter := counter - 1;
    else
    {
        counter := clockRate
        state := !state;
    }
}
```


IO - UART

 

IO - UART

 

IO - UART

 

0

1

IO - UART

serial.dhl

```
circuit UARTTx(int symbolTime)
{
    port out bool tdx;
    port in bits!8 enq;
    port in bool valid;
    port out bool ready;

    reg bits buffer = 0b11111111;
    reg uint state = 10;
    reg uint counter = symbolTime;

    txd := buffer[0];

    ...

    ready := state == 0;
}
```

IO - UART

```
if(state == 0)
{
    if(valid)
    {
        buffer := enq ~ 0;
        counter := time;
        state := 10;
    }
}
else
{
    if(count == 0)
    {
        buffer := 1 ~ buffer[9..1];
        counter := time;
        state := state-1;
    }
    else
        counter := counter-1;
}
```

IO - UART

serial.dhl

```
circuit UARTTx(int symbolTime)
{
    port out bool tdx;
    port in bits!8 enq;
    port in bool valid;
    port out bool ready;

    reg bits buffer = 0b1111111111;
    reg uint state = 10;
    reg uint counter = symbolTime;

    txd := buffer[0];

    ...
    ready := state == 0;
}
```

```
port Decoupled(T)
{
    port in bool valid;
    port out bool ready;
    port in T payload;
}
```

IO - UART

serial.hdl

```
circuit UARTTx(int symbolTime)
{
    port out bool tdx;
    port in Decoupled!(bits!8) enq;

    reg bits buffer = 0b1111111111;
    reg uint state = 10;
    reg uint counter = symbolTime;

    txd := buffer[0];

    ...

    enq.ready := state == 0;
}
```

IO - UART

```
if(state == 0)
{
    if(enq.valid)
    {
        buffer := enq.payload ~ 0;
        counter := time;
        state := 10;
    }
}
else
{
    if(count == 0)
    {
        buffer := 1 ~ buffer[9..1];
        counter := time;
        state := state-1;
    }
    else
        counter := counter-1;
}
```

IO - UART

serial.dhdl

```
port UARTPeripheral
{
    port in rxd;
    port out txd;
}

port UARTCtl
{
    port in Decoupled!(bits!8) enq;
    port out Decoupled!(bits!8) deq;
}

circuit UART(int symbolTime)
{
    port in UARTCtl ctl;
    port in UARTPeripheral pins;
    auto tx = new UARTRx!symbolTime;
    auto rx = new UARTRx!symbolTime;
    tx.txd <> pins.txd
    // ...
}
```


IO - UART

test-serial.dhdl

```
circuit TestSerial
{
    port in UARTPeripheral uartPins;


    auto uart = new UART!230400;
    uart.ctl.enq.valid := true;
    uart.ctl.enq.payload := 'D';
    uartPins.txd = uart.pins.txd;
}
```

IO - UART

 

A screenshot of a PuTTY terminal window titled "COM6 - PuTTY". The window has a white header bar with the title and standard window control buttons (minimize, maximize, close). The main area is a black terminal window. In the top-left corner of the black area, there is a single green square character. The rest of the window is empty.

10 - 7 segment

 

FPGA IO - 7 segment

sevensegment.dhdl

```
switch(digit)
{
    case 0x0: pins.segments := 0b1000000; break;
    case 0x1: pins.segments := 0b1111001; break;
    case 0x2: pins.segments := 0b0100100; break;
    case 0x3: pins.segments := 0b0110000; break;
    case 0x4: pins.segments := 0b0011001; break;
    case 0x5: pins.segments := 0b0010010; break;
    case 0x6: pins.segments := 0b0000010; break;
    case 0x7: pins.segments := 0b1111000; break;
    case 0x8: pins.segments := 0b0000000; break;
    case 0x9: pins.segments := 0b0011000; break;
    case 0xA: pins.segments := 0b0001000; break;
    case 0xB: pins.segments := 0b0000011; break;
    case 0xC: pins.segments := 0b1000110; break;
    case 0xD: pins.segments := 0b0100001; break;
    case 0xE: pins.segments := 0b0000110; break;
    case 0xF: pins.segments := 0b0001110; break;
}
```

FPGA IO - 7 segment


sevensegment.dhdl

```
switch(activeDigit)
{
    case 0: pins.anodes := 0b00000001; break;
    case 1: pins.anodes := 0b00000010; break;
    case 2: pins.anodes := 0b00000100; break;
    case 3: pins.anodes := 0b00001000; break;
    case 4: pins.anodes := 0b00010000; break;
    case 5: pins.anodes := 0b00100000; break;
    case 6: pins.anodes := 0b01000000; break;
    case 7: pins.anodes := 0b10000000; break;
}
```


FPGA IO - 7 segment

sevensegment.dhdl

 
```
switch(activeDigit)
{
    case 0: pins.anodes := 0b00000001; break;
    case 1: pins.anodes := 0b00000010; break;
    case 2: pins.anodes := 0b00000100; break;
    case 3: pins.anodes := 0b00001000; break;
    case 4: pins.anodes := 0b00010000; break;
    case 5: pins.anodes := 0b00100000; break;
    case 6: pins.anodes := 0b01000000; break;
    case 7: pins.anodes := 0b10000000; break;
}
```




IO - VGA

 


IO - VGA

 

IO - VGA

 


IO - Audio

 

IO - Audio

- Delta-sigma DAC

 


audio.dhdl

```
port out bool audio;  
  
reg uint!8 sample;  
reg uint!9 deltaSigma;  
  
deltaSigma := deltaSigma + sample;  
  
audio := deltaSigma[8];
```

Demo


- Let's build an arcade with these components
 - What game should we use?
 - Something somewhat related to D...

Demo

 

Demo
 
```
c:\arcadedbg>arcadedbg.exe --elf
WRITE 1000 - 1F8F0 (1000 - 1F8F0)
WRITE
*
WRITE 20000 - 2BCB0 (20000 - 2BCB0)
WRITE
*
CLEAR 2BCB0 - 34F5C
WRITE
*
WRITE 35000 - 13E800 (2C000 - 135800)
WRITE
*
```



Demo



Demo

- Not shown for lack of time:
 - SDRAM Controller
 - RISC-V CPU
 - Cache
- LDC2 compiled with RISC-V backend
 - Lots of issues here...

Thank you